

4.0 Boolean logic uses logical gates effectively.

4.1 Creates logic tables to identify basic arguments and explain their function.

Study pages 115 to 127 of the textbook.

1. Write the Boolean algebraic expression for the following logic circuit.

