



Department of Education, Sabaragamuwa/weekly school

week- March - 2

Subject-Information and Communication
Technology

Grade-13

Prepared by – Zonal Education
Office, Rathnapura.

1. A half – adder obtains two inputs A and B and gives outputs Sum and Carry.
 - 1.) Give truth table for the half-adder.
 - 2.) Draw the logic circuit for the half - adder with the outputs Sum and Carry in the same logic circuit.

2. A system controls the flow of vehicles through a barrier based on three lights A,B and C. When a light is red, the signal is 0. When a light is green, the signal is 1. The barrier will open when the output X is 1.

The barrier opens if either,

- Light A is red and lights B and C are both green.
 - Or
 - Light A is green and Lights B and C are both red.
- (i) Construct truth table for this system.
 - (ii) Derive a Boolean expression in SOP (Sum of Product) form.
 - (iii) Draw a logic circuit for the Boolean expression obtained in (ii) above.