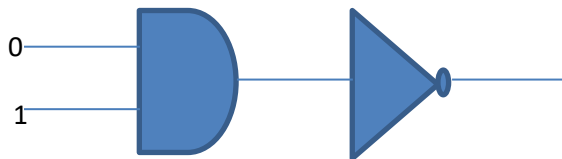





Unit 5 - Physical Computing

According to the given input, write the output of following logic circuits.

01.



02.

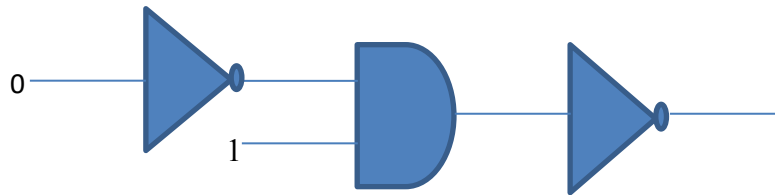

03.

