

පළාත් අධ්‍යාපන දෙපාර්තමේන්තුව
සබරගමුව - සනී පාසල

Grade- 8

Week 11

Subject - Science

Prepared by- Zonal Education Office
Embilipitiya

Electricity

- 1.What is series cell system? Draw the cell connection.
- 2.What is parallel cell system? Draw the cell connection.
- 3.What are the differences between series bulb system and parallel bulb system?
- 4.Using the circuit symbols for bulb, electric cell, switch, and connecting wires draw the circuit diagram for electric torch.
5. Give the examples for simple electric circuit.
- 6.Draw the following using the circuit symbols.

3 series cells	3 parallel cells	3 series bulb	3 parallel bulbs