

පළාත් අධ්‍යාපන දෙපාර්තමේන්තුව  
සබරගමුව - සනී පාසල

Grade- 8

Week 12

Subject - Science

Prepared by- Zonal Education Office  
Embilipitiya

## Electricity

1. Write short notes .

- Tap key
- Plug key
- Variable resistor

2. What is light dependent resistor?

3. Fill in the blanks using the given words.

(Switch, Electrical source, Parallel, close, electric source, voltage, series, electric current)

1. Flow of an electric charges is known as an .....
2. The path of an electric current is called an .....
- 3..... is supplied by an ..... to flow an electric current.
4. A ..... can be used to open or ..... a circuit when necessary.
5. There are two types of connecting components to a circuit. They are ..... and .....

