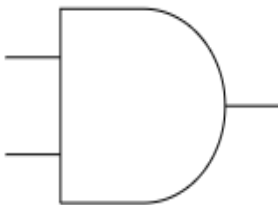4.0 Boolean logic uses logical gates effectively.

4.1 Creates logic tables to identify basic arguments and explain their function.

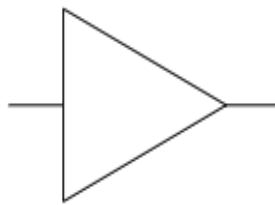**Study pages 115 to 126 of the textbook.**

1. Introduce logic circuits

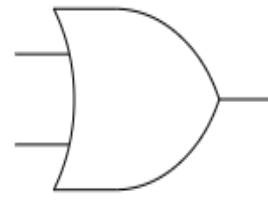2. Name the basic logic gates below and draw their truth tables.

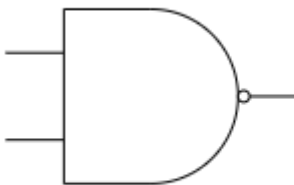A   B   C
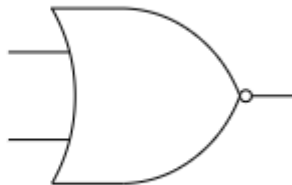
3. Name the compact logic gates below and draw their reality tables.

D   E